



## **1.Introduction to VLSI**

#### 1.1 Overview

- VLSI (Very-Large-Scale Integration) is the process of creating integrated circuits by combining thousands to millions of transistors on a single chip.
- This allows for complex and powerful electronic circuits to be miniaturized.
- VLSI is widely used in processors, memory chips, and advanced digital devices.

### 1.2 Evolution of VLSI

- First Functioning Point Contact Transistor was built in the year 1947
- Metal Oxide Semiconductor Field Effective Transistor (MOSFET) was built in the year 1959
- SSI: Small-Scale Integration with a few transistors per chip.
- MSI: Medium-Scale Integration, increasing to hundreds of transistors
- LSI: Large-Scale Integration, reaching thousands of transistors per chip.
- VLSI: Very-Large-Scale Integration, with millions of transistors on one chip.

### 1.3 VLSI Design Flow

- System Specification
- Architectural Design
- Functional Design
- Logic Design
- Ciruit Design
- Physical Design
- Fabrication
- Packaging & Testing

## 2.Digital world

## 2.1 Digital Design

- Digital design involves creating circuits that process digital signals.
- It uses binary logic (0s and 1s) for computations and data handling.
- Common elements include logic gates, flip-flops, and registers.
- Digital design is foundational for computers, processors, and digital devices.

## 2.2 Digital System

- A digital system processes and stores information in binary format.
- It consists of components like logic gates, memory units, and processors.
- Digital systems are reliable, precise, and programmable.
- Examples include computers, calculators, and digital communication devices.

## 2.3 Number System

- Binary Number System
- Decimal Number System
- Octal Number Syste
- Hexadecimal Number System





#### 2.4 Number Base Conversion

- Any to Binay (Positional Power)
- Decmal to Any (Using LCM)
- Grouping (Binary to Octal or Hexadecimal)

### 2.5 Binary Addition & Subtraction

- Binary addition involves adding bits and carrying over when the sum exceeds 1 (1+1 = 10).
- Binary subtraction requires borrowing when subtracting 1 from 0 (1-0 = 1, 0-1 = borrow).
- 1's complement is used by inverting bits to perform subtraction.
- 2's complement involves inverting bits and adding 1 for subtracting signed numbers.

### 2.6 Further Reading - Number Systems

- BCD Code
- Excess-3 Code
- Gray Code
- Weighted & Non Weighted

## **3.Logic Design**

## 3.1 Overview

#### **Digital Signals**

- High Level = +5v
- Low Level Ov

#### **Positive Logic**

- High = 1/True
- Low = 0/False

## **Negetive Logic**

- High = 0/False
- Low = 1/True

#### 3.2 Boolean Algebra Identities

- Identity Law
- Null Law
- Complement Law
- Idempotent Law
- Domination Law

## Properties

- Commutative Property
- Associative Property
- Distributive Property
- Complementary Property
- Idempotency Property
- Absorption Property





## 3.3 Logic Gates

- Logic gates perform basic operations on binary inputs (0s and 1s).
- AND: Outputs 1 when all inputs are 1.
- OR: Outputs 1 when at least one input is 1.
- NOT: Inverts the input (0 to 1, 1 to 0).
- NAND: Outputs 0 only when all inputs are 1.
- NOR: Outputs 0 when at least one input is 1.
- XOR: Outputs 1 when inputs are different.
- XNOR: Outputs 1 when inputs are the same.

#### **Universal Gates**

- NAND Gate: Can create any other gate by combining NANDs.
- NOR Gate: Can form all basic gates through NOR combinations.
- Both NAND and NOR are called universal gates for their versatility in digital circuits.

## 4. Combinational Circuits

## 4.1 Adder & Subtractor Circuits

#### **Basic Function**

• Adder and subtractor circuits are fundamental arithmetic circuits in digital electronics, used to perform addition and subtraction operations on binary numbers.

#### Half adder

• A half adder is a simple circuit that adds two single-bit binary numbers and outputs a sum and a carry, though it does not handle carry-in from previous stages.

#### Full adder

• A full adder adds three binary bits (including carry-in from previous addition) and outputs a sum and carry, making it suitable for multi-bit binary addition when chained together.

#### Subtractor circuit

• A binary subtractor circuit performs subtraction of two binary numbers, and often uses two's complement representation to handle both positive and negative numbers.

#### Combined adder-subtractor

• A single circuit can be designed to function as both an adder and subtractor by incorporating control signals to toggle between addition and subtraction modes.

#### Applications

• These circuits are essential in digital systems like calculators, computers, and microprocessors for performing arithmetic operations and are foundational for arithmetic logic units (ALUs).





## 4.2 Multiplexer & De-Multiplexer Circuits

## Multiplexer (MUX)

• A multiplexer is a digital circuit that selects one input from multiple inputs and forwards it to a single output based on control signals, enabling efficient data routing.

## **Control Signals**

• Multiplexers use control signals to select which input to forward, with the number of control lines determined by the number of inputs (e.g., a 4-to-1 MUX requires 2 control lines).

## Demultiplexer (DEMUX)

• A demultiplexer takes a single input and directs it to one of multiple outputs, based on control signals, distributing data to different channels.

### Data management

• MUX and DEMUX circuits are crucial for data management in communication systems, allowing multiple signals to be transmitted over a single line and then distributed as needed.

## Applications

• Used in digital electronics, MUX and DEMUX circuits are essential in systems like digital TVs, data routing, and information processing in computer systems.

### **Foundational Role**

• Multiplexers and demultiplexers are foundational components in the design of complex digital circuits, aiding in efficient data flow and signal control within processors, memory units, and communication networks.

## 4.3 Encoder and Decoder Circuits

## Encoder

• An encoder is a digital circuit that converts an active input signal into a coded output, typically reducing multiple input lines into fewer output lines, often in binary form.

## **Binary Encoding**

• Encoders are commonly used to convert input signals into binary codes, providing a more compact representation of information for easier processing.

## **Priority Encoder**

• A priority encoder assigns priority to inputs, encoding only the highest-priority active input, which is useful in interrupt handling in computer systems.

## Decoder

• A decoder performs the reverse function of an encoder, converting coded binary inputs back into specific outputs, allowing binary data to be decoded for various applications.

## **Control Signals**

• Decoders use control inputs to activate specific output lines, essential in memory addressing, display systems, and data routing in digital systems.

#### Applications

• Encoders and decoders are widely used in digital electronics, such as in communication systems, binary data conversion, memory address decoding, and interfacing with microcontrollers and processors.





### 4.4 Comparator Circuits

#### **Basic Function**

• Comparator circuits compare two input voltages or currents and output a signal indicating which input is higher, essential for decision-making in digital electronics.

### Types

• Comparators are commonly available as open-loop (non-feedback) circuits and include types such as inverting and non-inverting comparators.

### **Output Levels**

• The output of a comparator is usually binary, providing a high (1) or low (0) signal based on the comparison, making it ideal for threshold detection.

#### Applications

• Comparators are used in applications like analog-to-digital converters (ADCs), level sensing, zero-crossing detection, and pulse-width modulation (PWM) circuits.

### **Precision & Speed**

• Comparators are designed to provide quick response times and high accuracy, especially in applications requiring fast switching between states.

## **5.Sequential Circuits**

#### 5.1 Latches

- Latches are basic storage elements that hold a single bit of data.
- They are level-triggered and change output based on input when enabled.
- Common types include SR, D, and JK latches.
- Used in digital circuits to store and maintain data states.

## 5.2 Flip Flops

- SR Flip Flop
- JK Flip Flop
- D Flip Flop
- T Flip Flop

## 5.3 Shift Registers

- Shift registers store and shift data bits in a sequence.
- They move bits left or right with each clock pulse.
- Types include Serial-In Serial-Out (SISO) and Parallel-In Parallel-Out (PIPO).
- Commonly used in data storage, transfer, and manipulation.

#### 5.4 Counter

- · Counters are sequential circuits that count pulses.
- They can be binary, counting in binary sequence, or decimal.
- Types include synchronous and asynchronous counters.
- Used in timing, event counting, and frequency division.





#### 5.5 Finite State Machines (FSMs)

- FSMs are models of systems with a finite number of states.
- They transition between states based on inputs and conditions.
- Types include Mealy and Moore machines.
- Used in control systems, protocols, and digital logic design.

#### 5.6 Switch Debounce

- Switch debounce eliminates false signals from mechanical switch bouncing.
- It can be implemented in hardware (e.g., with capacitors) or software (e.g., delays).
- Debouncing ensures a single, clean signal for each button press.
- · Common in keyboards, buttons, and input devices to improve reliability.

### 5.6 Timing Analysis

- Timing analysis ensures that signals in a digital circuit meet required timing constraints.
- It involves checking setup, hold, and propagation delays in sequential circuits.
- Ensures that data is stable before and after clock transitions.
- Used to verify circuit performance and avoid timing violations.

## 6.Semiconductors

#### 6.1 Overview

- Semiconductors are materials with conductivity between conductors and insulators.
- They are key to electronic components like diodes, transistors, and integrated circuits.
- Silicon is the most common semiconductor material.
- Semiconductors enable control of electrical current in modern electronic devices.





## 6.2 N-Type & P-Type Semiconductors

## **N-Type Semiconductor**

• An N-type semiconductor is doped with elements that have more valence electrons than the semiconductor (usually phosphorus in silicon), creating extra free electrons that serve as charge carriers.

## **Electron Majority**

• In N-type semiconductors, the majority charge carriers are free electrons, which move towards the positive terminal under an electric field, contributing to electrical conductivity.

### P-Type Semiconductor

• A P-type semiconductor is doped with elements that have fewer valence electrons (such as boron in silicon), creating "holes" (missing electrons) that act as positive charge carriers.

### Hole Majority

• In P-type semiconductors, the majority charge carriers are holes, which are essentially the absence of an electron, and they move towards the negative terminal under an electric field.

### Formation of P-N Junction

• When N-type and P-type materials are joined, a P-N junction is formed, enabling the creation of diodes, transistors, and other semiconductor devices essential for electronic circuits.

### Applications

• N-type and P-type semiconductors are the building blocks for devices like diodes, transistors, and integrated circuits, used extensively in computers, solar cells, and other electronic components.

## 6.3 Transistors

#### **Basic Function**

• A transistor is a semiconductor device used to amplify or switch electronic signals, acting as a key building block in modern electronic circuits.

## Types

• There are two main types of transistors—bipolar junction transistors (BJT) and field-effect transistors (FE-T)—each with unique operating principles and applications.

## Switching & Amplification

• Transistors can function as switches, controlling the flow of current between two terminals, or as amplifiers, boosting the strength of weak signals.

#### Applications

• Transistors are essential in applications like signal processing, amplification in audio systems, logic gates in digital circuits, and power regulation in power supplies.

## Integration in ICs

• Transistors are the fundamental components in integrated circuits (ICs), enabling the development of complex microprocessors, memory chips, and other electronic devices.





## 7.Field Programmable Gate Array (FPGA)

#### 7.1 Overview

- FPGA (Field-Programmable Gate Array) is a flexible, reconfigurable hardware device.
- It consists of an array of programmable logic blocks and interconnections.
- FPGAs are used for custom hardware design and parallel processing tasks.
- They are commonly used in digital circuits, signal processing, and embedded systems.

### 7.2 Basic Architecture

- FPGAs have programmable logic blocks (CLBs).
- Configurable interconnects link the blocks.
- Input/output blocks (IOBs) handle external connections.
- · Programmable routing matrix enables flexible wiring.
- May include memory and DSP blocks.
- Configured via a bitstream.

## 7.3 Comparison of FPGAs with CPLDs, Microcontrollers and ASCIs Flexibility

• FPGAs offer high flexibility with programmable logic; CPLDs are less flexible; Microcontrollers and ASCIs are typically fixed.

#### Size and Complexity

• FPGAs handle large, complex designs; CPLDs are simpler; Microcontrollers are compact with limited complexity; ASCIs are custom-designed for specific tasks.

#### **Processing Power**

• FPGAs excel in parallel processing; Microcontrollers focus on sequential tasks; CPLDs offer moderate processing; ASCIs provide tailored power.

#### Reconfigurability

• FPGAs are fully reconfigurable; CPLDs are limited; Microcontrollers and ASCIs are generally fixed.

Speed

• FPGAs are the fastest; Microcontrollers are slower; CPLDs sit between them; ASCIs are optimized for specific tasks.

#### **Power Consumption**

• Microcontrollers consume the least power; CPLDs are more efficient than FPGAs, which consume more power.

#### Cost

• Microcontrollers and CPLDs are more cost-effective; FPGAs are more expensive; ASCIs vary in cost.

#### **Use Cases**

• FPGAs are used for high-performance tasks; Microcontrollers in embedded systems; CPLDs for simpler logic; ASCIs for custom applications.





## 8.Hardware Description LanguageS (HDL)

#### 8.1 Verilog HDL Overview

#### Hardware Description Language

• Verilog HDL is used to model digital systems, describing the behavior, structure, and timing of circuits in a textual form.

#### Simulation and Testing

• It allows for simulation and verification of digital designs before hardware implementation, ensuring functionality and performance.

### **Design and Synthesis**

• Verilog is widely used for both designing and synthesizing circuits, particularly in FPGA and ASIC development.

### C-like Syntax

• Verilog has a syntax similar to the C programming language, making it easier to learn for those familiar with programming.

### 8.2 Typical Design Flow

- Write Verilog code to define the design.
- Behavioural Description
- RTL Description (HDL)
- Functional Verification & Testing
- Logic Synthesis/Timing Verification
- Gatelevel Netlist
- Logic Verification & Testing
- Floor Planning Automatic Place & Route
- Physical Layout
- Layout Verification
- Implementation

## 8.3 Lexical Convention

- Lexical conventions define the basic syntax rules of a language.
- They specify valid identifiers, keywords, and literals.
- Whitespace is ignored except in string literals or comments.
- Comments are used for code annotations, usually starting with // or /\*.
- Symbols like =, +, and represent operators in the language.





## 8.4 Data Types

### Value Set

- It is used to represent signals that can hold a specific set of values.
- The most common value sets are used for signals that have multiple states, and Verilog provides several data types to represent these different sets

### Nets

- · It represent continuous connections and signal pathways between circuit elements
- They do not store values but instead carry signals based on input values from connected drivers, like combinational logic.
- Net datatypes are essential for modeling connections that respond continuously to input changes in combinational circuits.

#### Registers

- Registers (reg) store values in sequential logic, retaining state until updated.
- They work by holding data on a clock edge, useful for flip-flops and memory.
- Assigned in always and initial blocks, updating based on triggers.

### Vector

- A multi-bit data type, specified by a range (e.g., reg [7:0]), used to represent buses and multi-bit signals.
- Declared with a range, like [7:0], to specify bit-width and direction.
- Useful for handling binary data, signals, and registers of varying sizes.

## Integer

• A 32-bit signed data type used for variables, counters, and loops in procedural blocks.

#### Real

• Represents floating-point numbers for simulation purposes, but not synthesizable to hardware.

## Time

• A special datatype used to represent simulation time, typically in units of time like nanoseconds or picoseconds.

## Arrays

- Arrays in Verilog store multiple values of the same data type, accessed by index.
- Declared with dimensions, like reg [7:0] my\_array [0:3], to specify size.
- Commonly used for memory storage, lookup tables, or grouped data signals.

## Memories

- Used to represent arrays of data elements, allowing for storage and retrieval of multiple values in a structured way.
- These are especially useful for modeling RAM, ROM, and other forms of storage within digital systems

## Parameter

• Defines constants that are set at compile-time, commonly used for configuration in modules.

## Strings

• Represents an array of characters, used in simulation for text handling and debugging, but not synthesizable.





## 8.5 System Tasks & Compliers

## System Tasks

- Displaying Information
- Monitoring Information
- Stopping and Finishing a Simulation

## **Compiler Directives**

- Define
- Include

## 8.6 Modules & Ports

- Modules in Verilog define the design blocks or components of a circuit.
- Each module has ports (input, output, inout) for communication with other modules.
- Ports enable data flow into and out of the module, making designs modular.
- Modules can be instantiated within other modules, allowing hierarchical design.

## 8.7 Verilog Modeling

## **Behavioral Modeling**

• Describes the functionality of a design at a high level using constructs like always blocks, if statements, and loops, focusing on what the design does rather than how it is implemented.

## **Dataflow Modeling**

• Uses continuous assignments and operators (e.g., assign statements) to describe the flow of data between signals, emphasizing how data moves through the design.

## Structural Modeling

• Builds a design by interconnecting lower-level modules, representing the hardware structure directly, similar to a schematic or physical connections.

## **Gate-Level Modeling**

• Describes the circuit using basic logic gates (e.g., and, or, not) and flip-flops, providing a very detailed, low-level representation of the design.

## Switch-Level Modeling

• Models circuits at the transistor level using switches (pmos, nmos), capturing the exact behavior of MOS-FET-based designs and suitable for low-level simulations.

## Mixed-Modeling

• Combines behavioral, dataflow, and structural modeling techniques within a single design to optimize performance and flexibility in different parts of a Verilog module.

## 8.8 Basic Circuits written in Verilog

- Verilog describes digital circuits using modules, defining structure and behavior.
- Circuits can be designed at various abstraction levels: behavioral, dataflow, or structural.
- Supports combinational (logic gates) and sequential circuits (flip-flops, registers).
- Simulations verify functionality, while synthesis converts code to hardware.





## 8.9 Design Methodologies

- Top-Down Design
- Start with a high-level overview, then break down into detailed components.
- Bottom-Up Design
- Begin with basic components, combining them to build complex systems.
- HDL-Based Design
- Use Hardware Description Languages like Verilog or VHDL to model circuits.
- Simulation and Testing
- Verify functionality through simulations before hardware implementation.





## CAPSTONE PROJECTS

#### **1** Sequence Detector

- **FSM Design Principles**: Hands-on experience will be gained in designing and implementing finite state machines, enhancing understanding of sequential logic.
- Verilog Proficiency: Skills in Verilog coding will be improved, including state transitions and output generation, which are crucial for digital design.
- **Simulation and Testing:** The importance of simulation for verifying functionality and identifying errors will be learned, ensuring reliable performance before deployment.

#### 2 Traffic Light Controller

- Asynchronous Counter Design: Develop a solid understanding of asynchronous counter mechanisms, focusing on state transitions for traffic control.
- Verilog Coding Techniques: Enhance Verilog programming skills, particularly in managing timing and synchronization for effective traffic light sequencing.
- **System Simulation**: Emphasize the significance of thorough simulation to validate the traffic light controller's operation under different conditions.

#### **3** Vending Machine using Verilog HDL

- **Digital Design Understanding:** Gain insight into designing a complex digital system, managing transactions and product selection efficiently.
- Verilog HDL Proficiency: Improve skills in Verilog HDL for creating modules that handle product selection, payment processing, and change return.
- **Testing and Simulation**: Learn the importance of thorough simulation and testbench creation to validate system functionality and handle edge cases.

### LIVE PROJECT

- 1 16-Bit RISC Processor
  - **Processor Architecture Insight:** Gain valuable knowledge of RISC-V architecture, focusing on instruction sets and their execution in hardware.
  - Verilog Implementation Skills: Enhance Verilog skills through practical application in designing and integrating ALU, registers, and control units.
  - **Debugging and Verification**: Develop techniques for debugging and verifying processor functionality, ensuring accurate instruction execution and data handling.